

Verilog

RENZYM

Expanding Horizons

Overview

- Logic Design review
 - Basic Building Blocks
 - Design Examples: Incrementer, Fifo
- Verilog: Coding Basic blocks
 - Use of Modules
 - Gates, Mux/Demux, Registers
 - Data Values
 - Counter Example

Logic Design Review

Register Transfer Level
(RTL) Design


Logic Design

Basic building blocks for Logic design are



- Gates
- Muxes/Demuxes
- Registers/Memory
- Arithmetic Operations (Adder, Subtractor, Multipliers etc.)
- State machines
- Any combinations of Above



Gates


Inputs

 



Outputs

 
 


  

 

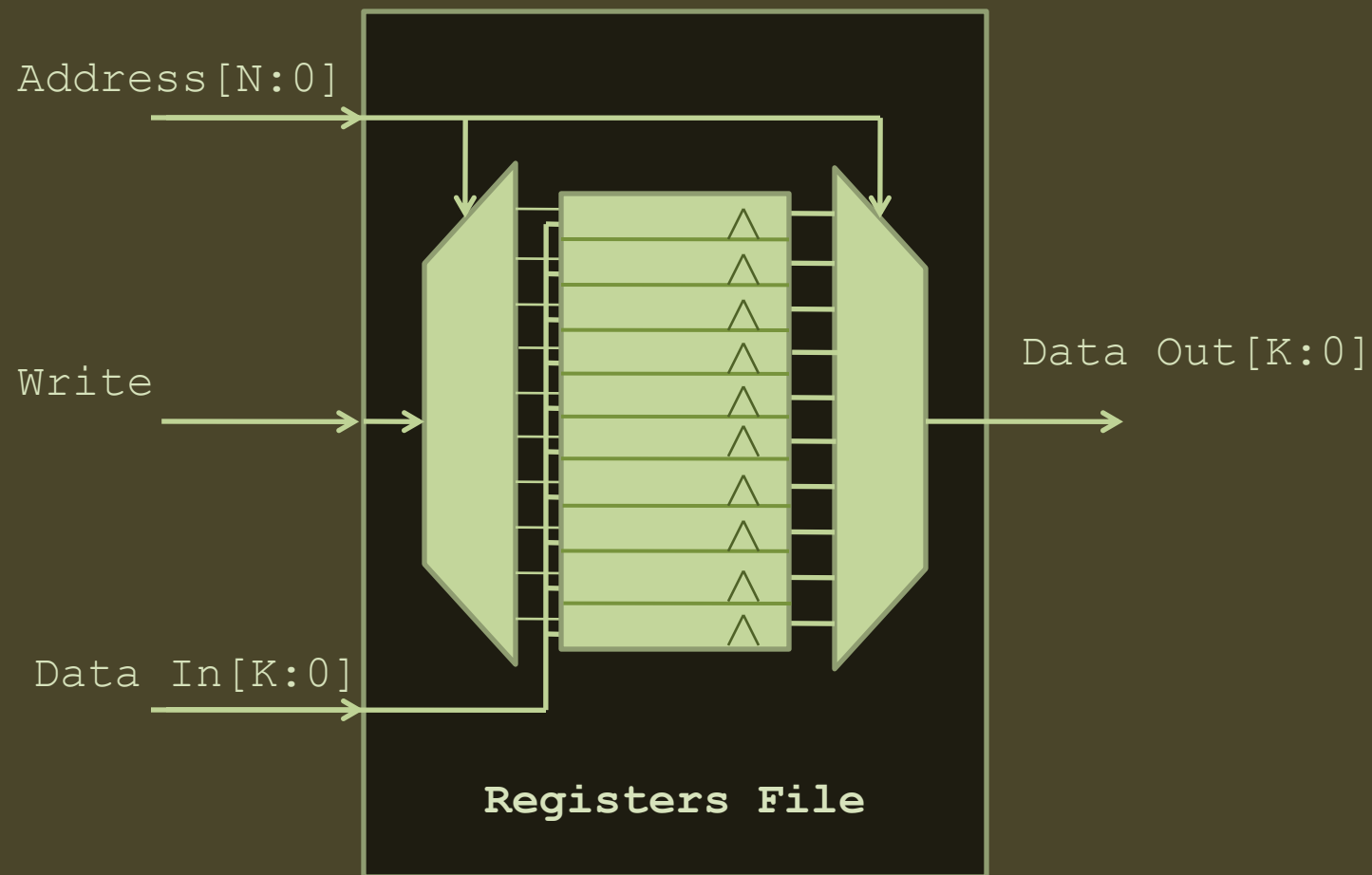

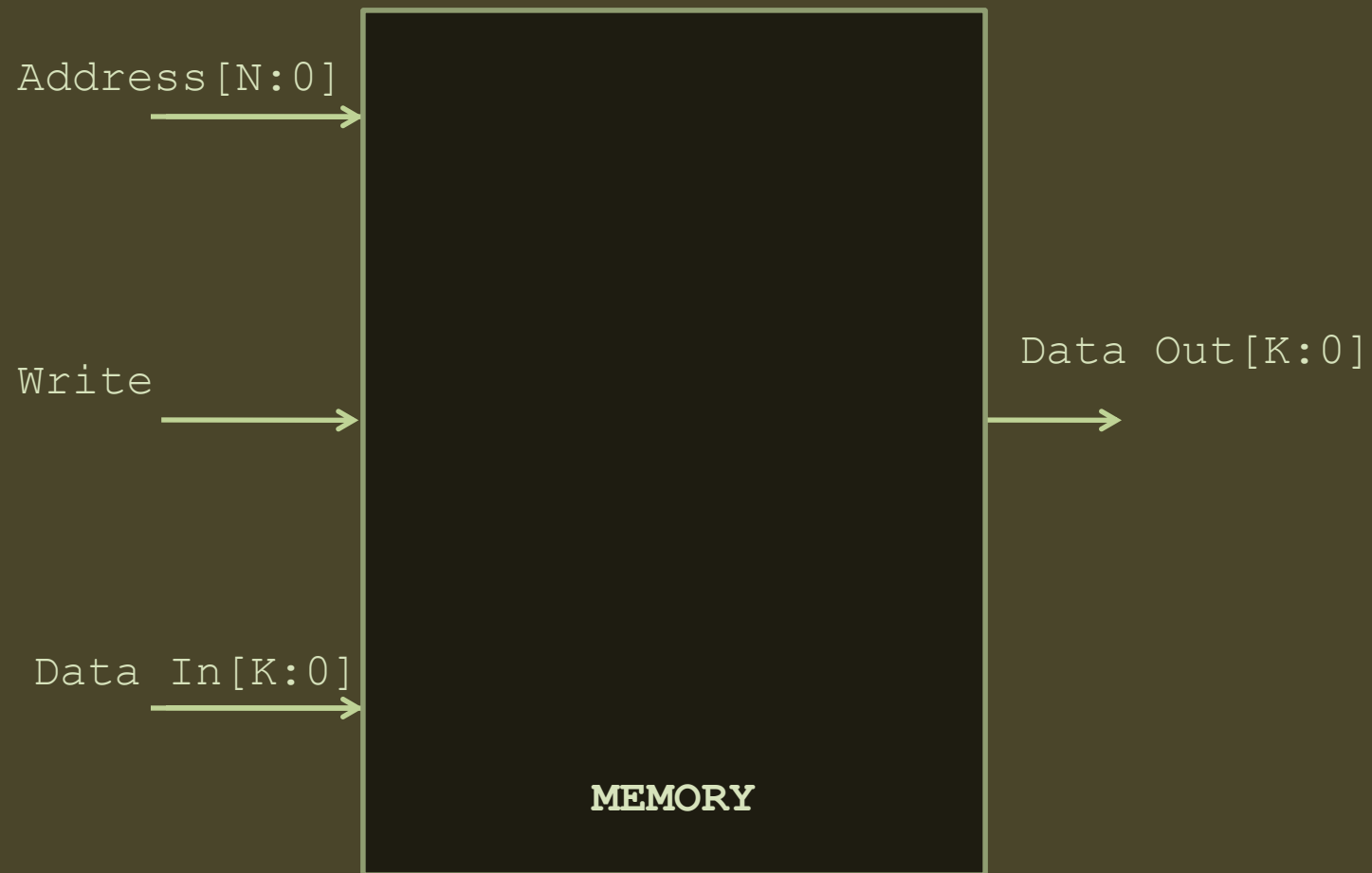

 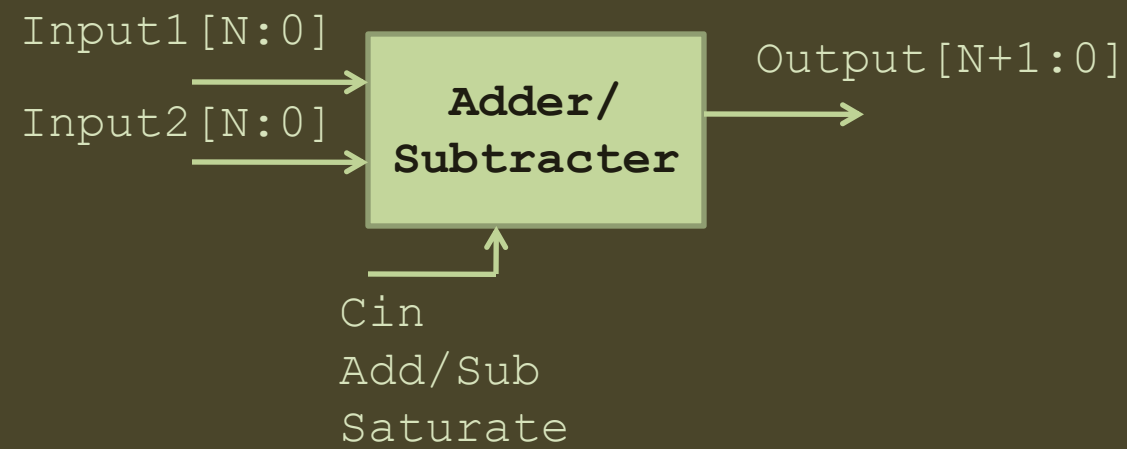

Making new Modules, Using Existing Modules

Design Examples


- **Example 1:**

- A simple decrementer capable of counting number of clock cycles down to zero.


- **Example 2:**



- A four deep FIFO

Decrementer

 



Four deep FIFO

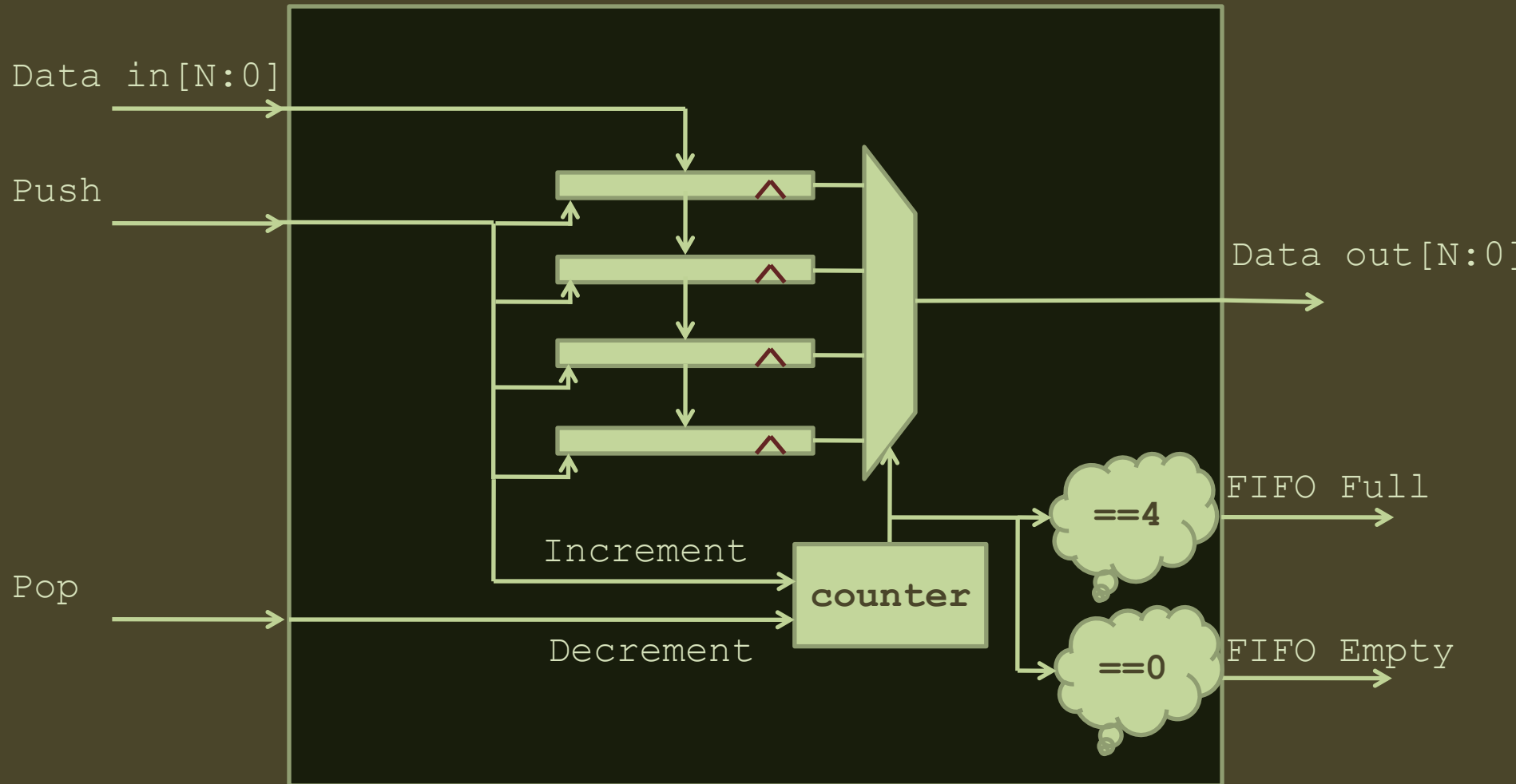

  


FIFO

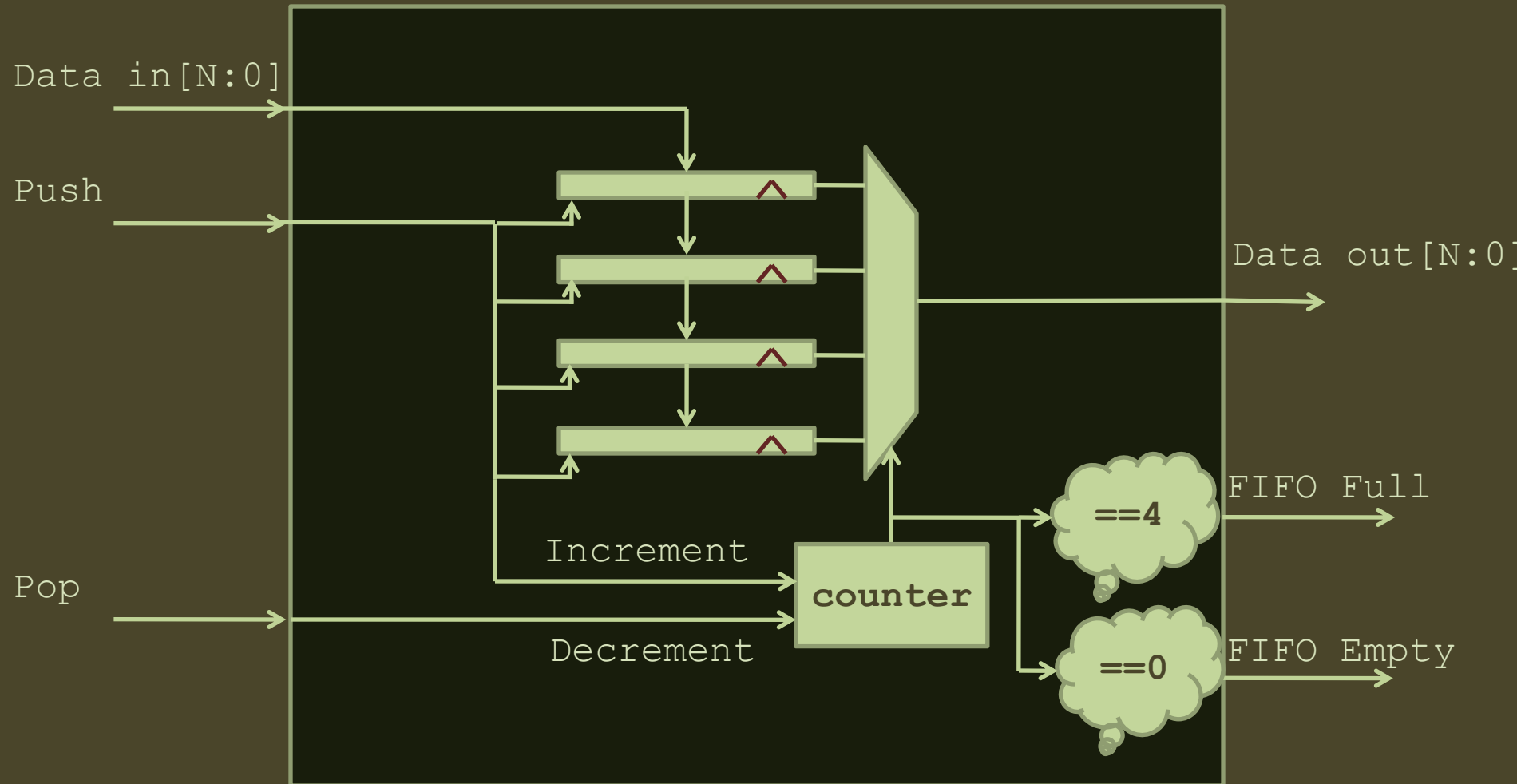

 

Other components

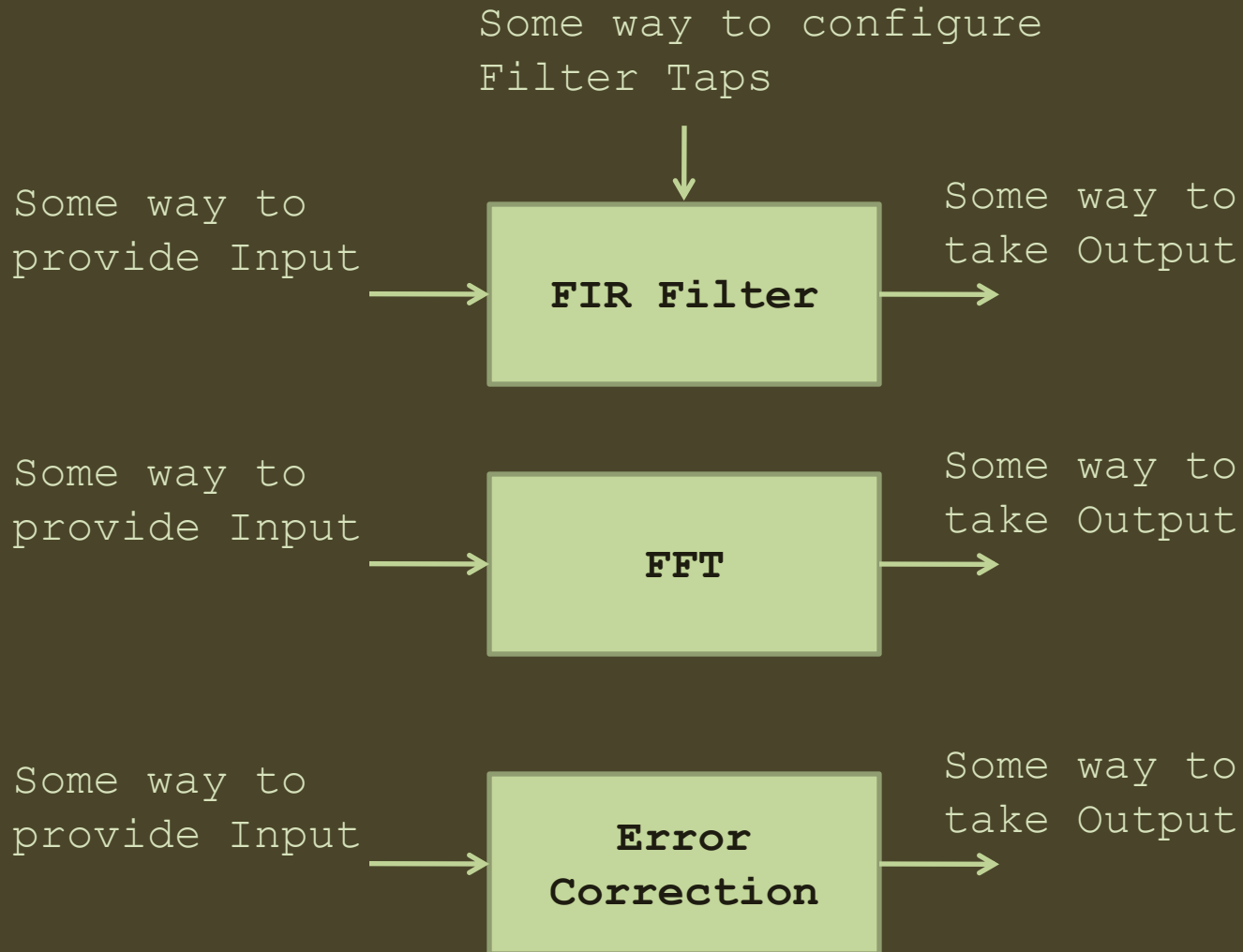

Verilog

RENZYM


Expanding Horizons

Verilog

Introduction to Modules

Verilog

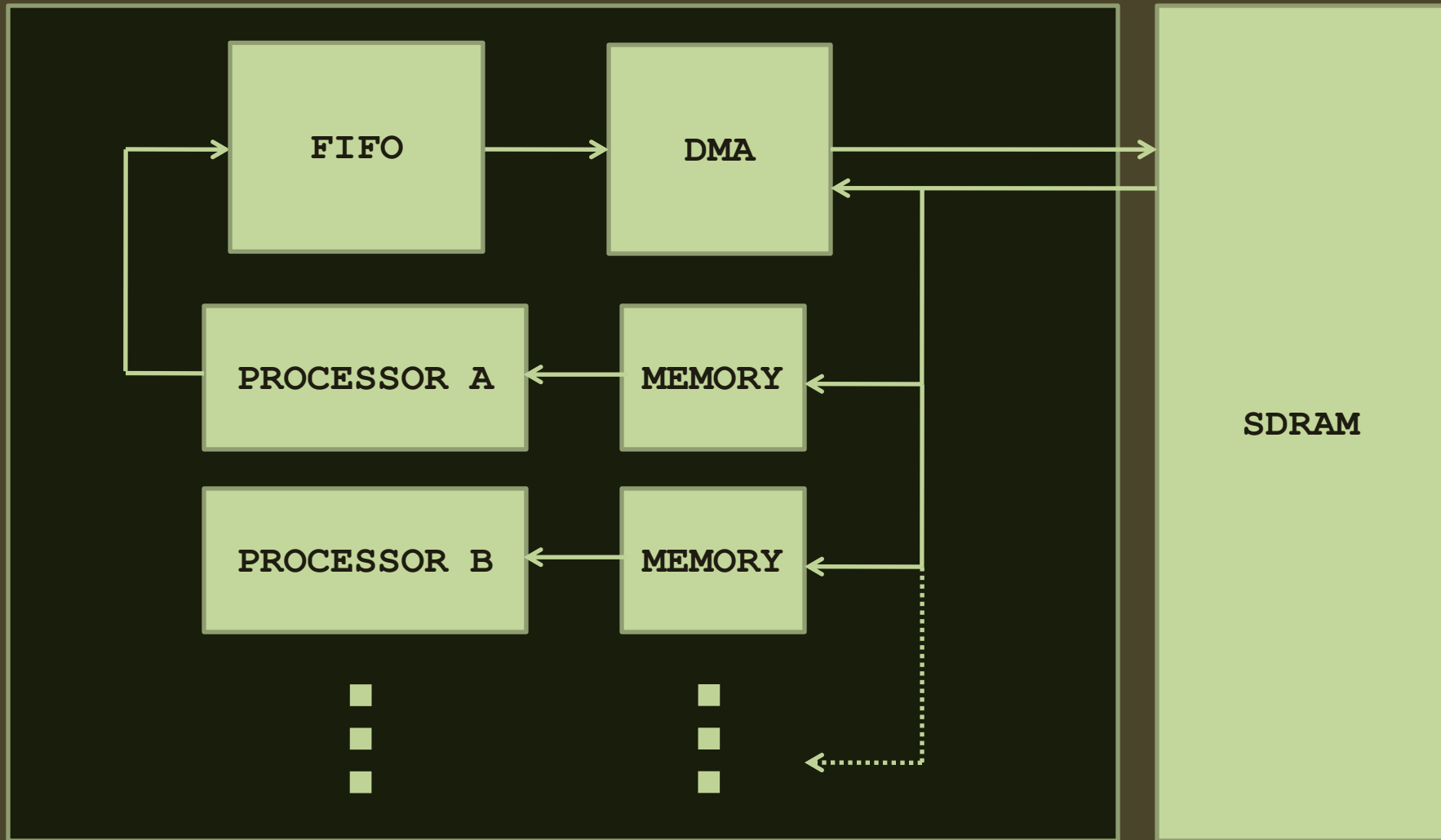Module: A reasonable size replicate-able block e.g. FIFO, counter and decrementer that we covered are good candidates.



fifo.v

data_in

push

pop

```
module fifo(  
    input [15:0] data_in,  
    input push,  
    input pop,  
    output [15:0] data_out,  
    output fifo_full,  
    output fifo_empty  
);
```

The code for modeling FIFO here

```
endmodule
```

data_out

fifo_full

fifo_empty

fifo.v

```
module fifo(  
  input  [15:0]  data_in,  
  input          push,  
  input          pop,  
  output [15:0]  data_out,  
  output         fifo_full,  
  output         fifo_empty  
);
```

The code for modeling FIFO here

```
endmodule
```

counter.v

```
module counter(  
  input          increment,  
  input          decrement,  
  output [3:0]   count  
);
```

Code for modeling Counter

```
endmodule
```



```
module counter(  
    input      increment,  
    input      decrement,  
    output[3:0] count
```

```
module fifo(  
    input  [15:0] data_in,  
    input          push,  
    input          pop,  
    output [15:0] data_out,  
    output          fifo_full,  
    output          fifo_empty  
);
```

The code for modeling FIFO here

```
endmodule
```

ling Counter

```
module counter(  
    input        increment,  
    input        decrement,  
    output[3:0]  count
```

```
    wire push;  
    wire pop;  
    wire [3:0] count;  
  
    counter counter_inst1(  
        .increment    (push),  
        .decrement    (pop),  
        .count        (count)  
    );
```

ling Counter

counter

Summary

- A block level hierarchy can be modeled as modules.
- Module is the basic building block.
- A module can be instantiated inside another module.
- Module can be replicated with a different instance name.

Verilog

RENZYM

Expanding Horizons

Verilog

Basic building blocks

Basic Building Blocks

Basic building blocks for Logic design are


- Gates
- Muxes/Demuxes
- Registers/Memory
- Arithmetic Operations (Adder, Subtractor, Multipliers etc.)
- State machines

What we are trying to do?

We are trying to model our building blocks using words and characters organized in a set of files


Modeling Gates

```
always @ (*)  
begin  
    a = b & c & d;  
end  
  
a = b | c | d;  
  
a = b ^ c ^ d;  
  
a = ~b;
```

 

Modeling Muxes/Demuxes
 
```
always @(*)
begin
    case(addr)
        2'd0: out = a;
        2'd1: out = b;
        2'd2: out = c;
        2'd3: out = d;
    endcase
end
```



Data Values

8' hXA

8' bXXXX_1010

8' hA

8' d10

8' b0000_1010

↑
Width

↑
Base Format


↑
(b,o,d,h)

↑
Underscores
are ignored

X's show don't
care values

Modeling Muxes/Demuxes

 
```
always @(*)  
begin  
    case(addr)  
        2'd0: out = a;  
        2'd1: out = b;  
        2'd2: out = c;  
        2'd3: out = d;  
    endcase  
end
```



DEMUX


Modeling Muxes/Demuxes
 
```
always @(*)
begin
  case(addr)
    2'd0: {a,b,c,d} = {in,3'd0};
    2'd1: {a,b,c,d} = {1'd0,in,2'd0};
    2'd2: {a,b,c,d} = {2'd0,in,1'd0};
    2'd3: {a,b,c,d} = {3'd0,in};
  endcase
end
```




DEMUX

concatenation

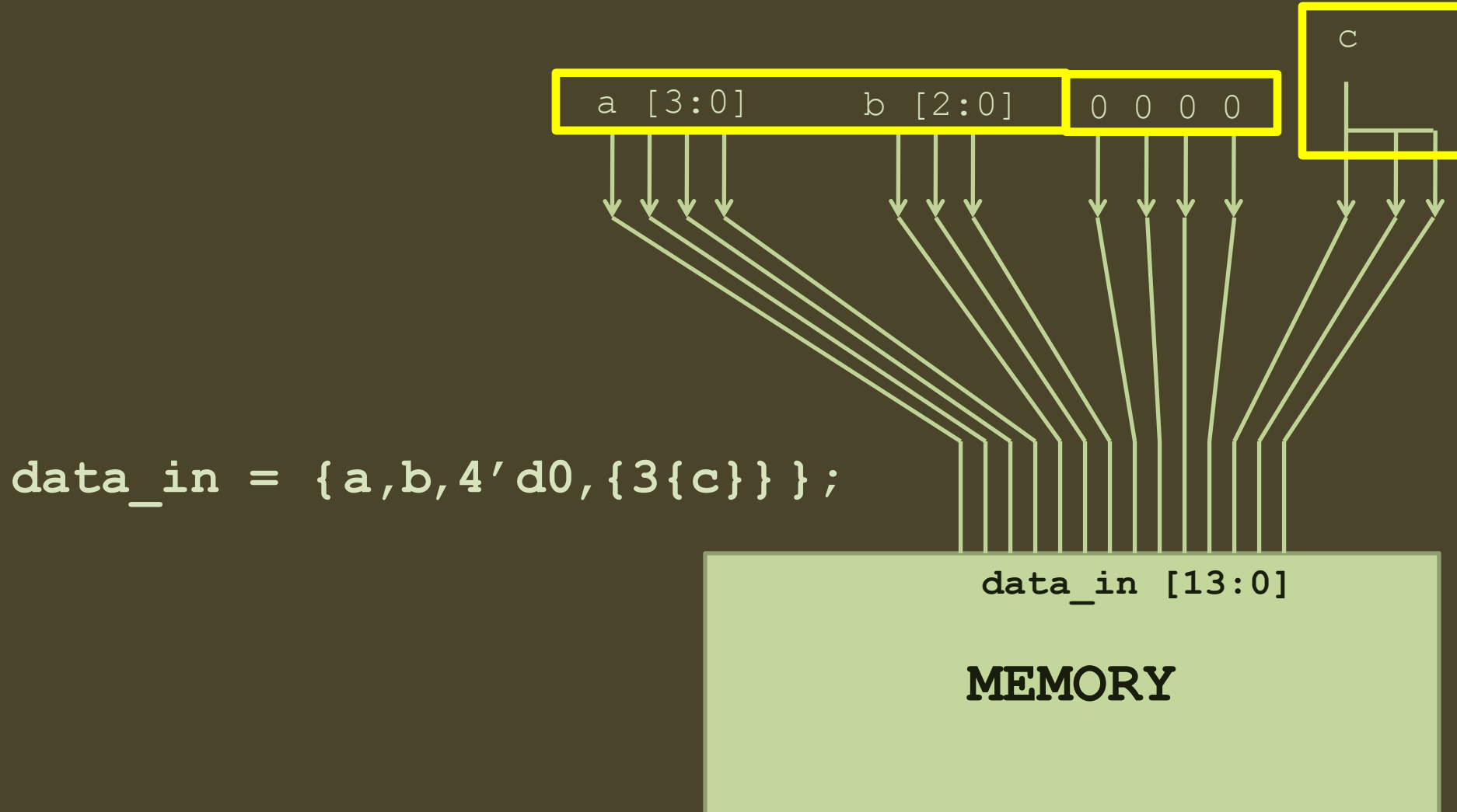


Modeling Muxes/Demuxes
 
```
always @(*)  
begin  
  case(addr)  
    2'd0: {a,b,c,d} = {in,3'd0};  
    2'd1: {a,b,c,d} = {1'd0,in,2'd0};  
    2'd2: {a,b,c,d} = {2'd0,in,1'd0};  
    2'd3: {a,b,c,d} = {3'd0,in};  
  endcase  
end
```



Modeling Registers


 
```
always@ (posedge clk)
begin
    if(reset)    reg_out <= #1 0;
    else        reg_out <= #1 reg_in;
end
```



Arithmetic Operations

```
always@ (*)  
begin  
    c = a + b;  
end
```

```
c = a - b;  
c = a * b;
```

 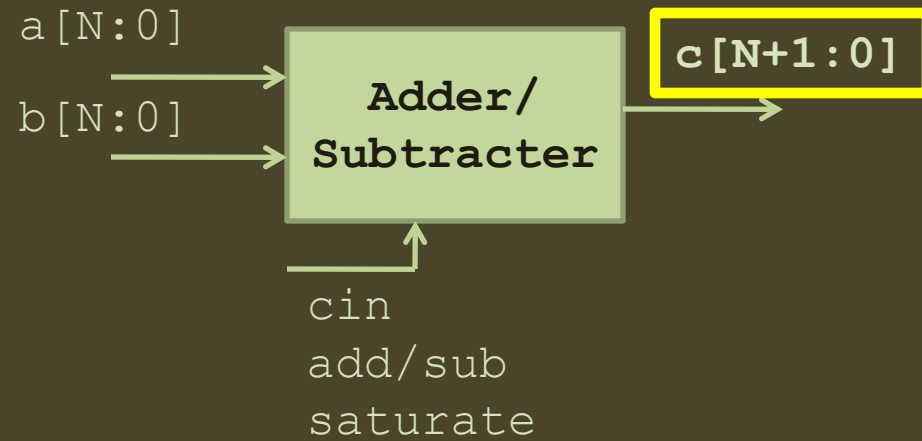

Declarations


```
reg [16:0] c;
```

```
wire [16:0] c;
```

```
always@(*)  
    c = a + b;
```

```
assign c = a + b;
```

 What about a & b?
Should they be
wire or **reg**?



```
always@(posedge clk)  
    c <= #1 a + b;
```

Verilog Coding

- Make a Design Diagram
- Code all the building blocks
 - Name the wires in the design diagram
 - Declare the module port list
 - Start coding the logic elements one by one
 - Declare Variables

```

module counter(
input      clk,
input      reset,
input      increment,
input      decrement,
output reg [3:0] count
);

    reg      enable;
    reg [3:0] mux_out;

    always@(*)
        enable = increment | decrement;

    always@(*)
    begin
        case(increment)
            1'b0: mux_out = count-1;
            1'b1: mux_out = count+1;
        endcase
    end

    always@(posedge clk)
    if(reset)
        count <= #1 0;
    else if(enable)
        count <= #1 mux_out;

endmodule

```

Example 1: counter.v

